



CAMBRIDGE INSTITUTE OF TECHNOLOGY

K.R. PURAM, BENGALURU-560036

Department of Basic Sciences

First Internal Assessment - Even Semester 2018-19

Sub. Name: Basic Electronics

Sub. Code: 18ELN24

Semester: II

Date: 02-04-2019

Time: 9:00 AM

Duration: 90 Minutes

Max. Marks: 30

[Instructions: Answer any two full questions as indicated below]

Sl. No.	QUESTIONS	COs	RBT Levels	Marks
1.	<p>a) List out the differences between diode and Zener diode.</p> <p>b) For a half wave rectifier, the input is from 30V transformer. The load and diode forward resistances are 100Ω and 10Ω respectively. Determine the I_{dc}, I_{rms}, P_{dc}, P_{ac}, η and γ.</p> <p>c) What is a voltage regulator? With a neat circuit diagram, explain the operation of a Zener voltage regulator with and without load.</p>	CO1 CO1 CO1	L1 L2 L2	03M 07M 05M
OR				
2.	<p>a) Define Forward bias and Reverse bias of a diode with circuit diagram.</p> <p>b) A half wave rectifier is fed from a supply of 230 V, 50 Hz with step down transformer of ratio 3:1 resistive load connected is $10K\Omega$. The diode forward resistance is 75Ω and transformer secondary is 10Ω. Determine the values of DC load current, DC load voltage, efficiency and ripple factor.</p> <p>c) Explain the operation of IC7805 voltage regulator.</p>	CO1 CO1 CO1	L1 L2 L2	03M 07M 05M
3.	<p>a) For E-MOSFET, find the value of I_D, if $I_{D(ON)} = 4mA$, $V_{gs(ON)} = 6V$, $V_T = 4V$ and $V_{gs} = 8V$.</p> <p>b) Write the structure of JFET and determine the expression for I_D and input resistance of the JFET.</p> <p>c) Explain the construction and working of enhancement type MOSFET.</p>	CO2 CO2 CO2	L1 L2 L2	03M 07M 05M
OR				

4.	a) Define the various JFET regions and its significance in the drain characteristics.	CO2	L1	03M
	b) With a neat diagram, explain the characteristics of Depletion type MOSFET.	CO2	L2	07M
	c) Explain the construction and operation of P-channel JFET with necessary diagram.	CO2	L2	05M

-----END-----